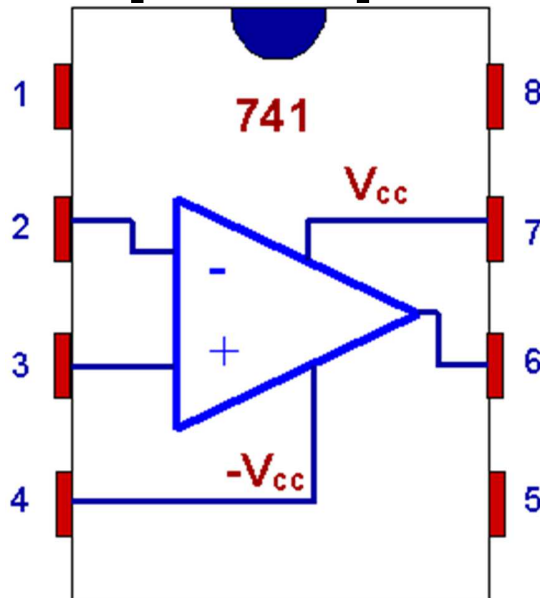


# Advanced Electronic Circuits

EAC215

## Basic Op-Amp Circuits



Name \_\_\_\_\_, \_\_\_\_\_ Class \_\_\_\_\_  
(Please print) Last Name First Name

**Objectives**

- To construct and test basic op-amp circuits

**Materials Required**

- LM741
- Discrete components as required

**Note**

Unless instructed otherwise, always assume a dual supply op-amp should be powered with  $\pm 12\text{V}$ .

**Procedure**

1. Design and sketch the circuit for an **inverting** op-amp with  $A_v = -100$ .
  
  
  
  
  
  
  
  
  
  
2. Construct the circuit on your breadboard and apply power.
3. Apply a signal of be 500mV @ 1kHz.
4. Ensuring your oscilloscope is AC coupled, sketch the input and output waveforms on oscilloscope graph paper. Clearly indicate the magnitudes of the input and output waveforms and their phase relationship.
5. Keeping  $V_{in}$  constant, increase the frequency to measure  $f_c$ .  $f_c = \underline{\hspace{2cm}}$
6. Sketch the frequency response graph on semi-log paper.
7. Demonstrate this circuit to the Instructor.

**Instructor Demo:** \_\_\_\_\_

8. Design and sketch the circuit for a **non-inverting** op-amp  $A_v = 101$ .



9. Construct the circuit on your breadboard and apply power.
10. Apply a signal of be 500mV @ 1kHz.
11. Ensuring your oscilloscope is AC coupled, sketch the input and output waveforms on oscilloscope graph paper. Clearly indicate the magnitudes of the input and output waveforms and their phase relationship.
12. Keeping  $V_{in}$  constant, increase the frequency to measure  $f_c$ .  $f_c = \underline{\hspace{2cm}}$
13. Demonstrate this circuit to the Instructor.

**Instructor Demo:** \_\_\_\_\_

14. What is the gain of a voltage follower \_\_\_\_\_
  15. What is the difference between a voltage follower and a buffer?
- 
- 

16. Design and sketch the circuit for a **voltage follower** op-amp.

17. Construct the circuit on your breadboard and apply power.
18. Apply a signal of be 1V @ 1kHz.
19. Ensuring your oscilloscope is AC coupled, sketch the input and output waveforms on oscilloscope graph paper. Clearly indicate the magnitudes of the input and output waveforms and their phase relationship.
20. Keeping  $V_{in}$  constant, increase the frequency to measure  $f_c$ .  $f_c = \underline{\hspace{2cm}}$
21. Sketch frequency response graph on semi-log paper.
22. Demonstrate this circuit to the Instructor.

**Instructor Demo:** \_\_\_\_\_